 


**Lab #2: Mux Design and Extension Unit Design**

**I. MUX Design**

**1. Requirement**

Design a 32-bit 2-to-1 multiplexer using behavioral or data flow implementation style (your choice). Data inputs and output must be 32-bit vectors. Source selection is 1-bit. If source selection is 0, then source A will be selected as output, otherwise source B. The block diagram of this component is as below:



The interface can be as below:

```
entity MUX_32Bits_Design is
    port(
        S: in std_logic;
        A: in std_logic_vector(31 downto 0);
        B: in std_logic_vector(31 downto 0);
        Y: out std_logic_vector(31 downto 0)
    );
end MUX_32Bits_Design;
```

**2. Pre-lab**

- Study and analyze the working of a MUX (How it works and its purposes)

**3. Lab**

- Write the VHDL code for this MUX design
- Simulate using Xilinx ISE simulator

**4. Deliverables**

- VHDL program
- VHDL test bench with enough test cases
- Waveform with comments

## II. Extension Unit Design

### 1. Requirement

Design an extension unit which can perform zero-extension or sign-extension from 16-bit binary number to 32-bit. If sign control signal is 0, then your design will perform zero-extension. If signal control signal is 1, then sign-extension will be performed.

*Example of zero-extension:*      $X''0ABD'' \rightarrow X''00000ABD''$

$X''7ABD'' \rightarrow X''00007ABD''$

$X''9DE2'' \rightarrow X''00009DE2''$

$X''8F2D'' \rightarrow X''00008F2D''$


*Example of sign-extension:*      $X''0ABD'' \rightarrow X''00000ABD''$      (positive number since MSb = '0')

$X''7ABD'' \rightarrow X''00007ABD''$      (positive number since MSb = '0')

$X''9DE2'' \rightarrow X''FFFF9DE2''$      (negative number since MSb = '1')

$X''8F2D'' \rightarrow X''FFFF8F2D''$      (negative number since MSb = '1')

 The block diagram of this component is as below:



The interface can be declared as below:

```

entity ExtensionUnit_32Bits is
  port(
    Sign_Ctrl: in std_logic;
    Data_In:   in std_logic_vector(15 downto 0);
    Data_Out:  out std_logic_vector(31 downto 0)
  );
end ExtensionUnit_32Bits;
  
```

### 2. Pre-lab

- Study and analyze the working of a sign extension unit in computer architecture (use lecture note (chapter 2, chapter 4) in class for your reference)

### 3. Lab

- Write the VHDL code for this component
- Simulate using Xilinx ISE simulator

### 4. Deliverables

- VHDL program
- VHDL test bench with enough test cases
- Waveform with comments