 


## Lab #6: Memory Design

## I. ROM Design

## 1. Requirement

Design ROM that has 16 locations each 32 bits wide. The 16 locations have the values like 0xDEADBEEF, 0xCAFEFABE, 0xDEADFEED and so on of your choice. There will be a *chipselect* (CS) input that activates the chip. The address input to the chip is a *vector*. The output would also be a *vector* that should send out the data already initialized at the active clock edge, depending on the address input to the chip.



The interface can be as below:

```
entity ROM_32Bits_Design is
  port(
    Clk:      in std_logic;
    CS:       in std_logic;
    Address:  in std_logic_vector(3 downto 0);
    Data_Out: out std_logic_vector(31 downto 0)
  );
```

## 2. Pre-lab

- Study and analyze the working of a ROM
- Study how to do the type conversion in VHDL:
  - `std_logic_Vector`  $\Leftrightarrow$  signed/unsigned
  - signed/unsigned  $\Leftrightarrow$  integer
  - `std_logic_vector`  $\Leftrightarrow$  integer

## 3. Lab

- Write the VHDL code for this ROM design (*recommend using conversion functions located in `numeric_std` library for index conversion for array*)
- Simulate using Xilinx ISE simulator


## 4. Deliverables

- VHDL program
- VHDL test bench with enough test cases
- Waveform with comments

## II. RAM Design
 
### 1. Requirement

Write VHDL code for a RAM that has 16 locations each 32 bits wide. There will be a chipselect (CS) input that activates the chip. Another input to the circuit is an R/W which determines if the operation is a read or a write to the chip. The address input to the chip is a vector. The input and output would also be a vector(s) that should send and receive the data, depending on the address input to the chip.



The interface can be declared as below:

```

entity RAM_32Bits is
  port(
    Clk: in std_logic;
    CS: in std_logic;
    R_W: in std_logic;
    Address: in std_logic_vector(3 downto 0);
    Data_In: in std_logic_vector(31 downto 0);
    Data_Out: out std_logic_vector(31 downto 0)
  );

```

### 2. Pre-lab

- Study and analyze the working of a RAM

### 3. Lab

- Write the VHDL code for this RAM design design (*recommend using conversion functions located in `numeric_std` library for index conversion for array*)
- Simulate using Xilinx ISE simulator

### 4. Deliverables

- VHDL program
- VHDL test bench with enough test cases
- Waveform with comments

## III. Bonus points (15 points): Optional

### 1. Requirement

Design a RAM with 32 locations each 32-bits wide by connecting 2 previous RAM designs together.

*Hint: use **port map** statements as introduced in lab#4, **MUX** and necessary logical gates to connect previous RAM design.*