


## Lab #10 (Final Project): 32-bit ALU Design

### 1. Requirement

Design a 32-bit ALU which can perform arithmetic and logic operations:

- The design has two 32-bit inputs, input A and input B: they are unsigned binary number
- The design must be able to perform:
  - Addition, increment, decrement and transfer (arithmetic operations)
  - AND, OR, NOT, XOR (logical operations)
  - Right shift, left shift (shift operations)
- The design must have 4-bit select line called Operation Select, which would direct the unit as to which operation to perform
- The unit has a Carry-in and also a Carry-out.

 The block diagram of this ALU is as shown below:



The interface of this design is as below:

```
entity ALU_32Bits_Design is
    port(
        Reg_A      : in std_logic_vector(31 downto 0);
        Reg_B      : in std_logic_vector(31 downto 0);
        Op_Sel     : in std_logic_vector(3  downto 0);
        Carry_In   : in std_logic;
        Carry_Out  : out std_logic;
        ALU_Out    : out std_logic_vector(31 downto 0)
    );
end ALU_32Bits_Design;
```

The Function Table of this ALU is as shown in **Table 1**. The ALU performs different operations according to the select lines (operation selection), i.e. the Op\_Sel signal dictates the operation performed by the Unit.

**Table 1: Function Table**

Operation Select (Op_Sel)				Carry_In	Operation	Function
Op_Sel(3)	Op_Sel(2)	Op_Sel(1)	Op_Sel(0)			
0	0	0	0	x	ALU_Out = A	Transfer Reg_A
0	0	0	1	x	ALU_Out = A + 1	Increment Reg_A
0	0	1	0	x	ALU_Out = A - 1	Decrement Reg_A
0	0	1	1	0 or 1	ALU_Out = A + B + Carry_In	Addition
0	1	0	0	x	ALU_Out = NOT A	Not Reg_A
0	1	0	1	x	ALU_Out = A AND B	Reg_A and Reg_B
0	1	1	0	x	ALU_Out = A OR B	Reg_A or Reg_B
0	1	1	1	x	ALU_Out = A XOR B	Reg_A xor Reg_B
1	0	x	x	x	ALU_Out = Shift A to the right by amount of bits defined by B	Right shift for Reg_A
1	1	x	x	x	ALU_Out = Shift A to the left by amount of bits defined by B	Left shift for Reg_A

## 2. Pre-lab

- Study the concept of an ALU

## 3. Lab

- Write the VHDL code for this unit
- Simulate using Xilinx ISE simulator

## 4. Deliverables

- VHDL program
- VHDL test bench with enough test cases which cover all the operations of this design
- Waveform with comments
- A Formal Lab Report

## 5. Guidelines

- The students are expected to record their Prelab/Design work in the Lab Journal
- In addition to turning in the Lab notebook, you are required to submit a Formal Lab Report
- The reports are individual, even though you work in teams.

## 6. Guidelines

- Working ALU Implementation: 50 points
- Good test-bench: 20 points
- Well-structured code including meaningful comments: 15 points
- Good lab report: 15 points